

**LM22670,LM22671,LM22672,LM22673,LM22674,
LM22675,LM22676,LM22677,LM22678,LM22679,
LM25005,LM3578A,LM5000,LM5001,LM5002,
LM5005**

*Application Note 1889 How to Measure the Loop Transfer Function of Power
Supplies*



Literature Number: SNVA364

How to Measure the Loop Transfer Function of Power Supplies

National Semiconductor
Application Note 1889
Frederik Dostal
October 14, 2008




Introduction

The regulation characteristics of most power management circuits are defined by the converter loop transfer function which can be plotted in a Bode plot. This representation of the gain of the loop as well as of the phase shift of the loop taken over frequency gives valuable information about the speed of the control loop and stability of the power supply. A Bode plot is ideally measured with a network analyzer but can also be obtained with very simple equipment available in most labs.

This tutorial will show how to measure the critical points of a bode plot with only an audio generator (or simple signal generator) and an oscilloscope. The method will be explained in an easy to follow step-by-step manner so that a power supply designer can start performing these measurements in a short amount of time.

Step 1: Setting up the Circuit


The first step is to break the loop of the power supply in order to have a point to inject a small signal and also to measure the signal going into the loop as well as coming out of the loop. Usually, the loop is broken at the low impedance output node above the high side feedback resistor in the feedback path. For a good injection point, one side of the node should be high impedance and one side should be low impedance. The injection point selected offers this combination. *Figure 1* shows a typical step down switch mode regulator schematic with the required measurement setup.

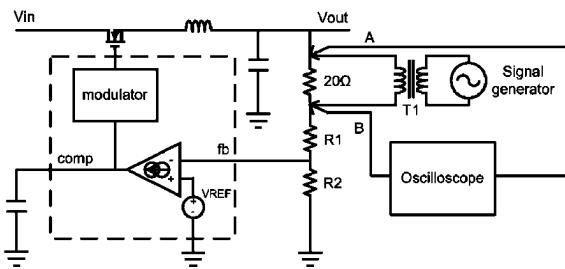

30075301

FIGURE 1. Measurement Setup

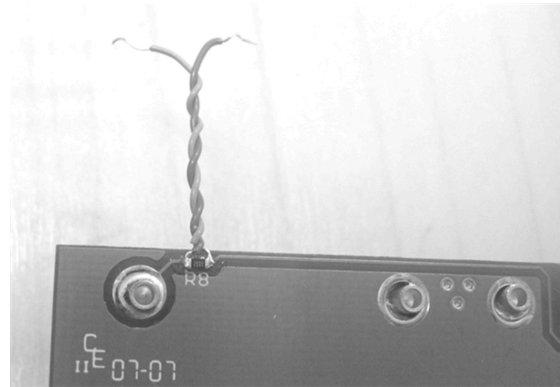To electrically separate the measurement points, A and B, a small resistance should be put in the feedback path. A good value is a 20Ω resistor. With such a resistor the adjusted output voltage will be negligibly influenced but the nodes to inject a small signal and measure the system are established.



30075302

FIGURE 2. Suggested Preparation of the Board


Any RC phase lead network which might exist in parallel with the $R1$ feedback resistor should stay in parallel with $R1$ and not be modified by the introduction of the 20Ω resistor.

A sound mechanical measurement structure is shown in *Figure 2*. The feedback path is broken on the PCB and a 20Ω resistor is soldered on the PCB. Some of evaluation boards may already have the spot for the stability measurement resistor prepared. On other boards it is relatively easy to cut the feedback trace on the PCB and reconnect it through a 20Ω resistor. For the connection of the two voltage probes as well as the signal injection cables a twisted cable as shown in *Figure 2* is very useful. Such a small twisted pair works very well for minimizing noise pickup which is critical for a good measurement. The tight connected twisted cable can be run for about two inches without a problem. Such a connection will help with the mechanical stress coming from the voltage probes as well as the signal injection connector while not influencing the measurement due to the tight twisting of the wires. The voltage probe ground connections should be connected at one ground connection on the power supply board. *Figure 3* shows the two scope probe connections to the board.

Step 2: The Injection Transformer

The injected signal has to be a small signal in relation to the output voltage. The injected signal should not be allowed to change the large signal behavior of the power supply, yet has to be large enough, so that it can be recognized once it travels around the loop. However it must not cause the loop to change its behavior. For example, some devices have output over voltage protection thresholds reflected at the feedback pin which should not be triggered due to the injected signal. A typical injected sine wave signal should be between 30mV and 100mV across the measurement resistor as described in step one. The exact value changes depending on the gain of the system and will vary with frequency. Start with a smaller signal first and then increase the signal if needed in order to see the injected signal. This will ensure that the signal is still considered a small signal in the application. The injection transformer is mostly used so that there is no DC connection from the tested power supply to the signal generator. There

are special transformers for such measurements available, which offer a very flat voltage transmission over a wide frequency band. When sweeping the frequency automatically such as with a network analyzer, the flat gain can be beneficial. For most applications and especially when the frequency of the injected signal is changed manually, the voltage transmission characteristic of the transformer can be balanced by changing the amplitude at the signal or audio generator. Then a transformer can be used which does not show a flat voltage transmission curve such as a very low cost standard transformer intended for a 110V to 12V off-line conversion. *Figure 3* shows such a transformer. In the schematic of *Figure 1*, *Figure 6* and *Figure 7* the transformer is labeled T1.

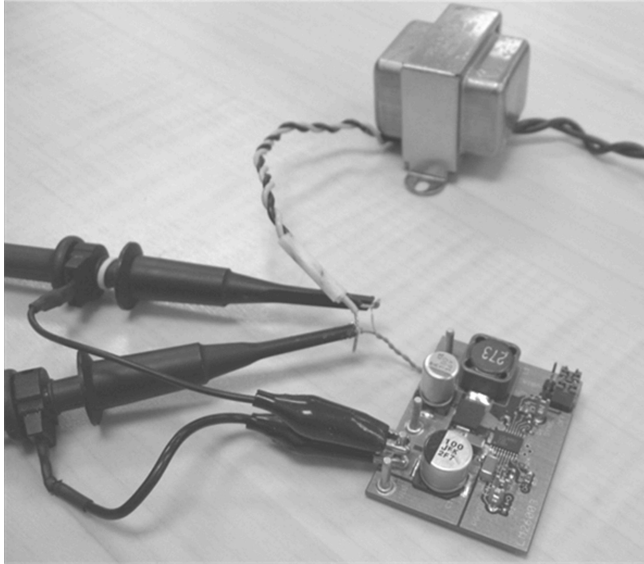

30075303

FIGURE 3. Setup of Injection Transformer and Scope Probes on a Switch Mode Power Supply Circuit

Step 3: Preparing the Signal Generator

The signal generator should provide a sine wave signal and the output should be connected to the 110V input side of the injection transformer. Then the output voltage of the injection transformer should be adjusted with the amplitude setting on the signal generator. This should be tested at different frequencies so that the amplitude on the signal generator can be adjusted to not drive the power circuit into non-linear operation. The DC offset of the output signal of the signal generator should be set to 0V since only the AC is coupled through the injection transformer.

Step 4: Hooking up the Oscilloscope

The oscilloscope may be analog or digital. It is important to have two calibrated scope probes with the same attenuation to simplify the measurement. Adjust both channels to the highest resolution possible and set AC coupling.

In order to avoid switching noise filling the oscilloscope screen and to focus on the waveform of interest, set the scope to bandwidth limiting. To get a well triggered picture of the sine waves one can trigger off a third channel which is attached to the signal generator. Triggering directly on channel A or channel B might be difficult due to the high frequency switching

noise pickup. When triggering on the signal generator directly, such problems are avoided. Also, this way the trigger will not have to get readjusted with changing amplitudes of channel A and B.


Step 5: Preparing the Power Supply

The power supply has to be put in the condition in which the stability test should be performed. This means powering up the board and attaching a load to the output. *Figure 3* does not show these cable connections to keep the picture simple. It is always a good idea to perform a stability measurement with different load and line conditions. At low output loads most power supplies will go into discontinuous current conduction mode which exhibits different loop characteristics. Also in voltage mode converters without input voltage feed forward, the loop characteristics will change with input voltage. Before a measurement can be taken, make sure to attach the signal injection transformer across the frequency injection resistor of the power supply and to attach the two voltage probes of channel A and B. The ground of both scope probes should be attached to a common ground connection on the power supply under test.

Step 6: Taking the Measurement

After setting up the equipment and powering everything up, the scope will probably show one line on one channel and a sine wave on the other channel. If there is no sine wave visible, either the scope is not set to the highest amplitude resolution (typically 20 mV per division) or the amplitude of the signal generator is set too low. Once a sine wave is visible, changing the frequency of the signal generator will lead to a change in amplitude on channel A and channel B. There will be a certain frequency when the sine waves of channel A and channel B have the same amplitude. This is the point where the gain of the loop is 1. The amplitude of the signal injected into the system is the same as the amplitude of the signal after being fed through the loop. The frequency set by the signal generator at which this happens is the frequency of the 0dB crossover of the system.

Figure 4 shows channel A and channel B on the oscilloscope screen when both waveforms have the same amplitude. This is the 0dB frequency.

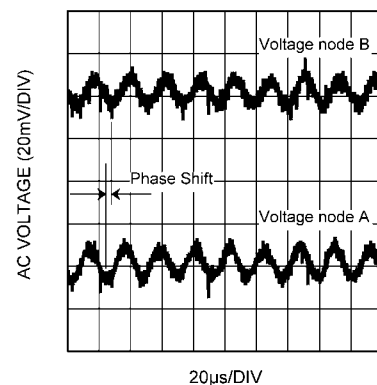

30075304

FIGURE 4. Measurement Showing 0dB Crossover

Typically, the two sine waves are phase shifted to each other. The amount of phase difference of the two signals is the phase margin at the 0dB crossover frequency. Besides the 0dB crossover point, other measurement points at lower fre-

requencies may be taken. The amplitude difference between channel A and channel B gives the gain at the frequency the signal generator is set to. The table below helps with the voltage difference and the corresponding value in dB according to the formula: $\text{dB} = 20\log A/B$.

TABLE 1. Commonly Used dB Values

dB level	Voltage ratio
-30dB	0.03162
-20dB	0.1
-10dB	0.3162
-3dB	0.7071
0dB	1
3dB	1.414
10dB	3.162
20dB	10
30dB	31.62

In order to take a full bode plot, the signal generator frequency is swept and at different points the gain as the amplitude relationship between the two channels and the phase shift are measured. Depending on the oscilloscope used for the measurement and the gain of the loop, it might be very difficult to see points of the bode plot with very large or very small gain. For 30dB for example, it is quite difficult to see a voltage relationship between channel A and B of a factor of about 32. For typical designs the most important points of a bode-plot such as the 0dB crossover point can easily and relatively accurately be measured. At high gain frequencies, it might be difficult to see the exact dB value, but a quantitative observation such as 'the gain is very high and probably above 30dB' can easily be made.

Loop measurements can only be taken successfully on a design which does not oscillate or is not in some sort of hysteretic over voltage protection mode. To achieve a stable design for measurements to be taken, one can use the following trick on current mode control designs. Place a large capacitance from the compensation pin to ground in designs where the error amplifier is a transconductance amplifier and from the compensation pin to the FB pin in designs where the error amplifier is a standard voltage to voltage error amplifier. A capacitor value of 1 μF will typically work well. It will set a pole at very low frequencies and force the gain to drop quickly so that the 0dB crossover is at a very low frequency as well. In current mode control designs, the phase margin at very low frequencies is usually enough to yield a stable design. This way plant gain measurements can be performed.

This measurement is only good for getting a compensation to output plot showing the power stage transfer function. This transfer function helps when selecting the right compensation components for the loop.

Step 7: Analyzing a Bode Plot

The most important measurement is the 0dB crossover of the gain. It provides information about the bandwidth of a power supply as well as the phase margin of a system.

System bandwidth can be considered as a combination of the level of DC gain as well as the frequency of the 0dB crossover. When looking at the phase shift of channel A versus channel B at this frequency, one measures the phase margin of the system which is used as an indicator of the stability margin of a power supply. Depending on how conservative a design is, a minimum phase margin of 45 to 50

degrees is necessary. More is better. *Figure 5* shows a typical bode plot taken with a network analyzer. It is taken from a current mode step down switch-mode regulator.

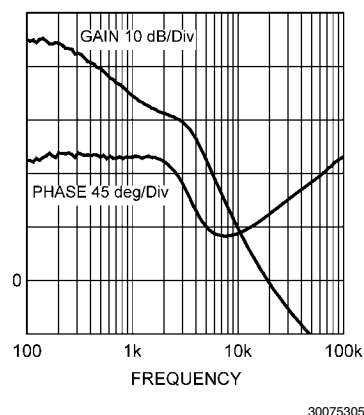


FIGURE 5. A Typical Bode Plot of a Step-Down Voltage Mode Switching Regulator

Also the frequencies of the plant poles and zeros can be found. This can help in selecting power stage components and compensation components.

Measuring the Plant Transfer Function

Besides the measurement setup of *Figure 1*, the channel which measures the injected signal going into the loop can also be attached to the compensation pin of a power supply design such as shown in *Figure 6*. In this setup the transfer function of the plant is measured without the influence of the compensation network attached to the compensation pin. This provides valuable information about the power stage. With this information it is easy to select optimized compensation components for a desired bandwidth and phase margin of a converter.


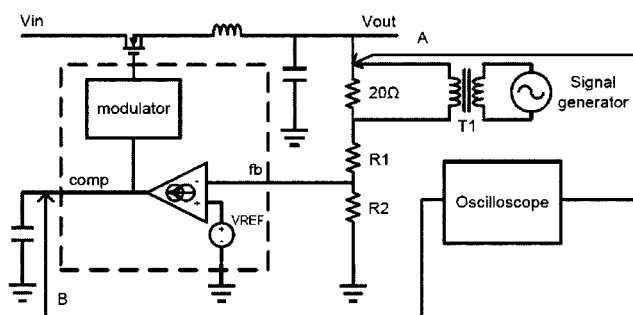


FIGURE 6. Setup to Measure the Plant of a Converter

Measuring in Cases with a Special Output Stage

As mentioned in step one of this document it is necessary to have an injection node in the loop which has a low impedance node on one side and a high impedance node on the other side for placing the injection resistor and attaching the voltage probes for the measurements. In typical fixed output voltage power supply designs, the best point to inject this signal is

between the output voltage and the high side feedback resistor. There are other designs where such a point is not available. One example is a fixed current source power supply to drive LEDs. The loop of interest is regulating a current through a string of LEDs. The current is measured with a high side current sense block which is sensing the LED current and is translating it into a voltage for the feedback node. To produce a place in the feedback path which has one side low-impedance and the other side high-impedance, the operational amplifier OP1 is added into the feedback loop as a buffer. If this amplifier is selected to be faster than half the switching frequency of the converter, the influence of this additional stage on the loop should be minimal. *Figure 7* shows such a loop stability measurement setup.

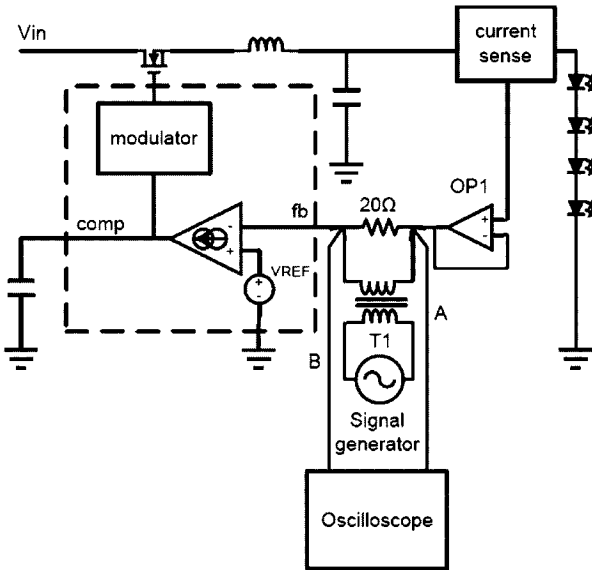

30075307

FIGURE 7. Setup with Artificially Generated Injection Node

Summary

A real network analyzer which sweeps the frequency of an injected signal automatically and computes the phase difference and the gain between channel A and channel B on the fly is nice to have and very convenient. However, measuring the control loop of a power supply can be done with basic lab equipment such as an oscilloscope, a simple signal generator and a very inexpensive standard transformer. In addition to line and load transient evaluation of a power supply, very useful data can be taken when performing these measurements such as the phase margin of a power supply design. When taking multiple measurements at different frequencies, a basic bode plot can be drawn without the use of expensive equipment. At the very least some sense of the accuracy of gain calculations can be obtained.

Notes

AN-1889

Notes

For more National Semiconductor product information and proven design tools, visit the following Web sites at:

Products		Design Support	
Amplifiers	www.national.com/amplifiers	WEBENCH	www.national.com/webench
Audio	www.national.com/audio	Analog University	www.national.com/AU
Clock Conditioners	www.national.com/timing	App Notes	www.national.com/appnotes
Data Converters	www.national.com/adc	Distributors	www.national.com/contacts
Displays	www.national.com/displays	Green Compliance	www.national.com/quality/green
Ethernet	www.national.com/ethernet	Packaging	www.national.com/packaging
Interface	www.national.com/interface	Quality and Reliability	www.national.com/quality
LVDS	www.national.com/lvds	Reference Designs	www.national.com/refdesigns
Power Management	www.national.com/power	Feedback	www.national.com/feedback
Switching Regulators	www.national.com/switchers		
LDOs	www.national.com/lido		
LED Lighting	www.national.com/led		
PowerWise	www.national.com/powerwise		
Serial Digital Interface (SDI)	www.national.com/sdi		
Temperature Sensors	www.national.com/tempsensors		
Wireless (PLL/VCO)	www.national.com/wireless		

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

Copyright© 2008 National Semiconductor Corporation

For the most current product information visit us at www.national.com



National Semiconductor Americas Technical Support Center
 Email: support@nsc.com
 Tel: 1-800-272-9959

National Semiconductor Europe Technical Support Center
 Email: europe.support@nsc.com
 German Tel: +49 (0) 180 5010 771
 English Tel: +44 (0) 870 850 4288

National Semiconductor Asia Pacific Technical Support Center
 Email: ap.support@nsc.com

National Semiconductor Japan Technical Support Center
 Email: jpn.feedback@nsc.com

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Transportation and Automotive	www.ti.com/automotive
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated